


1) 329394696 - 776 600

207


הרצון

1.6 100M 100M

1.2 100M

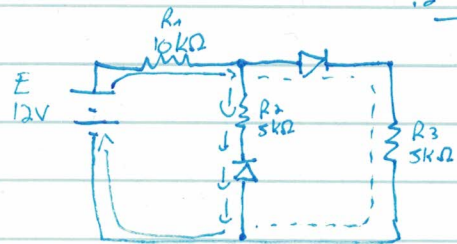

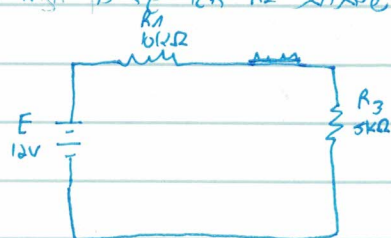הרצון 1.2 100M 100M (הרצון 1.2 100M 100M) הרצון 1.2 100M 100M



$$R_N = R_1 + R_3$$

$$R_N = 15k\Omega$$


$$I_N = \frac{12}{15} = 0.8A$$

$$(I_N = 0.8A) \quad I_{R1} = I_{R3} = 0.8A$$


$$U_{R1} = 12 \cdot \frac{3}{15} = 4V$$

$$U_{R3} = 12 \cdot \frac{10}{15} = 8V$$

1.3 100M

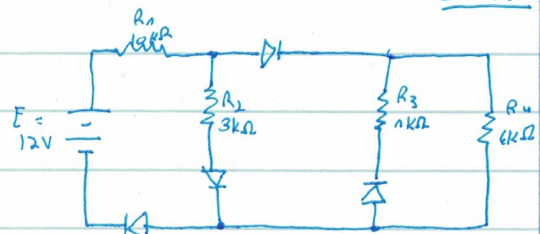

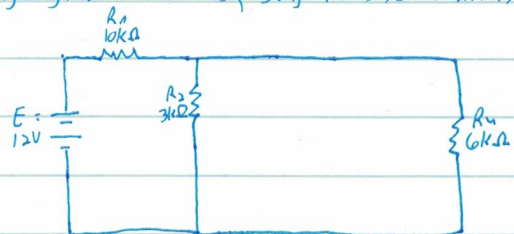הרצון 1.3 100M 100M (הרצון 1.3 100M 100M) הרצון 1.3 100M 100M



1.3 100M

$$R_{24} = \frac{0.3}{0.3} = 2k\Omega \quad (R_{24} = R_2 + R_4)$$

$$R_1 + R_{24} = 2 + 10 = 12k\Omega$$

1.3 100M

$$I_N = \frac{12}{12} = 1mA$$

(2)

207

$$I_{R_1} = I_{R_2,4} = 1 \text{ mA}$$

$$U_{R_1} = 1 \cdot 10 = 10 \text{ V}$$


$$R_{2,4} = 12 - 10 = 2 \text{ V} ; 2 \text{ k}\Omega$$

$$U_{R_2} = U_{R_4} = 2 \text{ V}$$

: p ה R_2 ו R_4 R_1 ו R_2


$$I_{R_4} = \frac{2}{6} = \frac{1}{3} \text{ mA} ; R_4 \text{ ה } R_2 \text{ ו } R_4$$

: 5 חלוקה

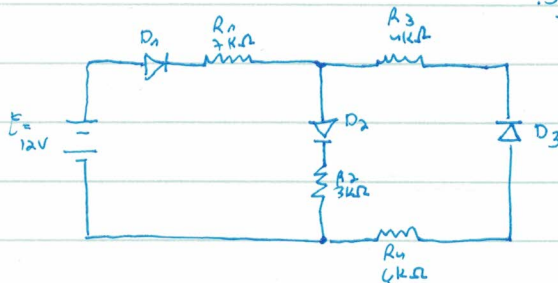

החלוקה D_1 ו R_1 D_2 ו R_2 D_3 ו R_3 D_1 ו R_1 D_2 ו R_2 D_3 ו R_3 D_1 ו R_1 D_2 ו R_2 D_3 ו R_3

: 5 חלוקה

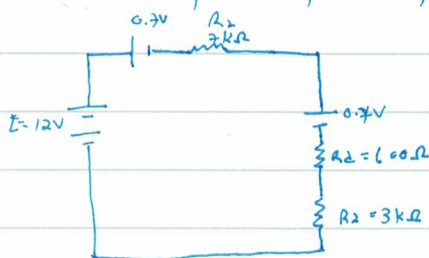


$$R_{\mu} = R_2 + R_3 + R_1$$

$$R_{\mu} = 10.6 \text{ k}\Omega$$

$$12 - 0.7 - 0.7 = 10.6 \text{ V} ; I_{\mu}$$


$$I_{\mu} = 1 \text{ mA}$$

: 5 חלוקה

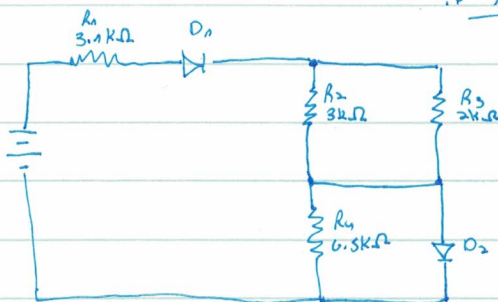

: 5 חלוקה

(3)

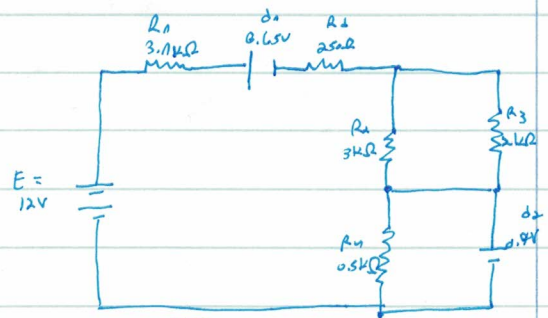

$$I_{R1} = \frac{9.3}{3.1} = 3\text{mA} \quad ; \quad U_{D1} = 0.65\text{V}$$

! D1 is in series with R1

$$U_{D1} = U_{D0} + (I_{R1} \cdot R_1)$$

3mA is the current through R1 and D1

$$U_{D1} = 0.65 + (3 \cdot 250) = 1.4\text{V}$$

$$R_{2,3} = \frac{R_2 \cdot R_3}{R_2 + R_3} \rightarrow R_{2,3} = \frac{3 \cdot 2}{3 + 2} = 1.2\text{k}\Omega \quad ; \quad \text{! } R_{2,3} \text{ is in series with } R_1$$


3mA is the current through R1 and R2,3

$$U_{R2,3} = 3 \cdot 1.2 = 3.6\text{V} \quad ; \quad \text{! } R_{2,3}$$


$U_{R1} = U_{D2} = 0.7\text{V}$ and D2 is in series with R3

$$E = U_{R1} + U_{D1} + U_{R2,3} + U_{D2}$$
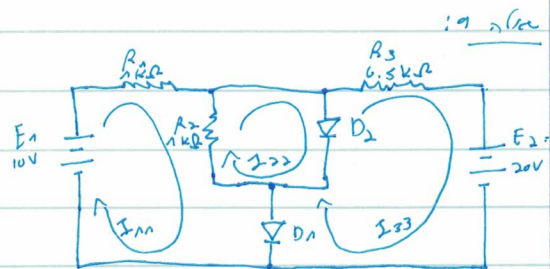
$$E = 9.3 + 1.4 + 3.6 + 0.7 = 15\text{V}$$


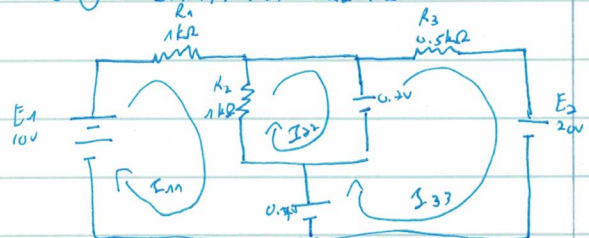
$$\text{KVL: } 10 = I_{R1} \cdot R_1 + I_{D1} \cdot R_1 + I_{D2} \cdot R_2$$



$$\text{I: } I_{R1} : E_1 = U_{D1} = I_{R1} (R_1 + R_2) - I_{D2} \cdot R_2$$

$$\text{II: } I_{D2} : -U_{D2} = I_{D2} \cdot R_2 - I_{R1} \cdot R_2$$

$$\text{III: } I_{D3} : U_{D2} - E_2 = I_{D3} \cdot R_3$$

$$\text{I: } 10 - 0.7 = 2I_{R1} - I_{D2}$$

$$\text{II: } -0.7 = I_{D2} - I_{R1}$$

$$\text{III: } 0.7 - 20 = 0.5I_{D3}$$

(b)

167

$$I_{33} = -\frac{37.2}{37.2} = -1$$

$$I_{11} = 8.6 = I_{11}$$

$$I_{11} = 8.6$$

$$I_{22} = -0.7 + I_{11}$$

$$I_{22} = 7.9$$

$$I_{R1} = I_{11} = 8.6 \text{ mA}$$

$$I_{R2} = I_{11} - I_{22} = 8.6 - 7.9 = 0.7 \text{ mA}$$

$$I_{R3} = I_{33} = 37.2 \text{ mA}$$

$$I_{R1} + I_{R2} = I_{R2} + I_{D2} \quad ; \text{KCL at node 1}$$


$$I_{D2} = 8.6 - 0.7 + 37.2 = 45.1 \text{ mA}$$

$$I_{D1} = I_{D2} = 45.1 \text{ mA}$$

$$I_{D1} = I_{R3} - I_{D2}$$

$$I_{D1} = 0.7 + 45.1 = 45.8 \text{ mA}$$

$$I_{D1} = 45.8 \text{ mA}$$

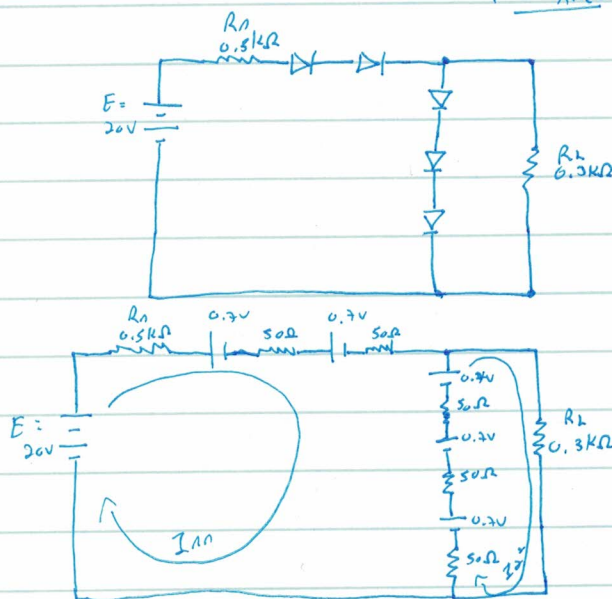

$$I: E - 0.7 - 0.7 - 0.7 - 0.7 - 0.7 = I_{11}(R_1 + 50 + 50 + 50 + 50 + 50) - I_{22}(50 + 50 + 50)$$

$$II: 0.7 + 0.7 + 0.7 = I_{22}(R_2 + 50 + 50 + 50) - I_{11}(50 + 50 + 50)$$

$$I: 16.5 = 0.75R_{11} - 0.15R_{22}$$

$$II: 2.1 = 0.45R_{22} - 0.15R_{11} \quad / \times 5$$

$$\begin{pmatrix} 0.7 = 0.15R_{22} - 0.05R_{11} \\ 17.2 = 0.7I_{11} \\ I_{11} = -17.9 \\ I_{22} = -44.1 \end{pmatrix}$$

(5)

P-3

$$II: 10.5 = 2.25 I_{22} - 0.75 I_{11}$$

$$I = II: 27 = 2.1 I_{22}$$

$$I_{22} = 12.857 \text{ mA}$$

: RL gain seen

$$V_{R1} = 12.857 \cdot 0.3: \text{ p.v.k. } \text{ p.v.k. } I_{R1} = I_{22}$$

$$V_{R1} = 3.85 \text{ V}$$